

**Western New England University**  
**College of Engineering**  
**ECE Department**  
**Microwave Engineering**  
**EE 414**  
**Spring 2024**  
**Design Project #3**  
**Due: April 17, 2024**

Name: Nittala Satya Surya Lakshmi Vasuki Siva Srinivas

#Id – 620094

Email – sn620094@wne.edu

References: \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

## Design Project #3

	Score	Max
Lumped Element Design		200
MATLAB LE Simulation		100
WG Iris Design		500
WG Iris (HFSS – V1)		200
WG Iris (HFSS – V2)		100
Summary Graphs		100
Table 1		100
Table 2		100
Presentation		200
Total		1600

1. Design a lumped element bandpass filter that meets the following performance specifications:
  - $f_0 = 22 \text{ GHz}$  .
  - $BW_f = 1 \text{ GHz}$  .
  - $RL \geq 26 \text{ dB}$  for  $f_L \leq f \leq f_H$  .
  - $IL \geq 20 \text{ dB}$  for  $f \leq f_{Ls}$  where  $f_{Ls} = 21 \text{ GHz}$  .
  - $IL \geq 35 \text{ dB}$  for  $f \geq f_{Hs}$  where  $f \geq f_{Hs} = 23.4 \text{ GHz}$  .
  - The source and load impedances of the filter are  $Z_0 = Z_0(f_0)$  (waveguide impedance). Assume that the waveguide is a WR42 waveguide ( $a = 10.6680 \text{ mm}$ ,  $b = 4.3180 \text{ mm}$ , and  $t_w = 1.0160 \text{ mm}$ ).
2. Using MATLAB and ideal lumped elements, simulate the BPF. Employ a frequency range of 20.5 GHz to 23.5 GHz.
  - On the same graph, plot  $|S_{11}|$  in dB and  $|S_{21}|$  in dB. Employ a frequency range of 20.5 GHz to 23.5 GHz and a range of -40 dB to 0 dB for  $|S_{k1}|$  .
  - Plot  $|S_{21}|$  in dB. Employ a frequency range of 21.4 GHz to 22.6 GHz and a range of -0.02 dB to 0 dB for  $|S_{21}|$  .
3. Convert the BPF into a waveguide inductive iris BPF. Assume that the waveguide is a WR42 waveguide ( $a = 10.6680 \text{ mm}$ ,  $b = 4.3180 \text{ mm}$ , and  $t_w = 1.0160 \text{ mm}$ ) and assume that each iris has a thickness of 1 mm ( $t = 1 \text{ mm}$ ). For each impedance inverter, determine a value for  $K/Z_0$ ,  $X_p/Z_0$ ,  $X_s/Z_0$ ,  $\psi$ ,  $\phi$ , and  $a_g$ . For each resonator, determine a value for  $d$  and  $\theta$  .
4. Using HFSS, simulate the waveguide inductive iris BPF. Employ a frequency range of 20.5 GHz to 23.5 GHz. In addition, assume that all metallic elements are perfect electric conductors.
  - On the same graph, plot  $|S_{11}|$  in dB and  $|S_{21}|$  in dB. Employ a frequency range of 20.5 GHz to 23.5 GHz and a range of -40 dB to 0 dB for  $|S_{k1}|$  .
  - Plot  $|S_{21}|$  in dB. Employ a frequency range of 21.4 GHz to 22.6 GHz and a range of -0.02 dB to 0 dB for  $|S_{21}|$  .


5. Using HFSS, simulate the waveguide inductive iris BPF with conductor loss. Employ a frequency range of 20.5 GHz to 23.5 GHz. In addition, assume that all metallic elements are copper.
  - On the same graph, plot  $|S_{11}|$  in dB and  $|S_{21}|$  in dB. Employ a frequency range of 20.5 GHz to 23.5 GHz and a range of -40 dB to 0 dB for  $|S_{k1}|$ .
  - Plot  $|S_{21}|$  in dB. Employ a frequency range of 21.4 GHz to 22.6 GHz and a range of -0.25 dB to 0 dB for  $|S_{21}|$ .
6. Summarize the results for the lumped element BPF (MATLAB), the waveguide inductive iris BPF (HFSS), and the waveguide inductive iris BPF with conductor loss.
  - On the same graph, plot  $|S_{21}|$  in dB, for the three cases. Employ a frequency range of 20.5 GHz to 23.5 GHz and a range of -40 dB to 0 dB for  $|S_{21}|$ .
  - On the same graph, plot  $|S_{21}|$  in dB, for the three cases. Employ a of frequency range 21.4 GHz to 22.6 GHz and a range of -0.25 dB to 0 dB for  $|S_{21}|$ .
  - On the same graph, plot  $|S_{11}|$  in dB, for the three cases. Employ a frequency range of 21.4 GHz to 22.6 GHz and a range of -40 dB to 0 dB for  $|S_{11}|$ .
7. Complete Table 1.
8. Complete Table 2.
9. Present the results from the design project into a well-organized presentation.

Table 1      Summary of the impedance inverter parameters.

$k, k + 1$	01	12	23	$\square$	$N_p, N_p + 1$	
$K_{k,k+1}/Z_0$				$\square$		$\Omega/\Omega$
$X_{p(k,k+1)}/Z_0$				$\square$		$\Omega/\Omega$
$X_{s(k,k+1)}/Z_0$				$\square$		$\Omega/\Omega$
$\Psi_{k,k+1}$				$\square$		$\circ$
$\phi_{k,k+1}$				$\square$		$\circ$
$a_g$				$\square$		mm

Table 2      Summary of the resonator parameters.

$k$	1	2	3	$\square$	$N_{\text{Resonators}}$	
$\theta_{k,k+1}$				$\square$		$\circ$
$d_k/\lambda_{g0}$				$\square$		$\Omega/\Omega$
$d_k$				$\square$		mm

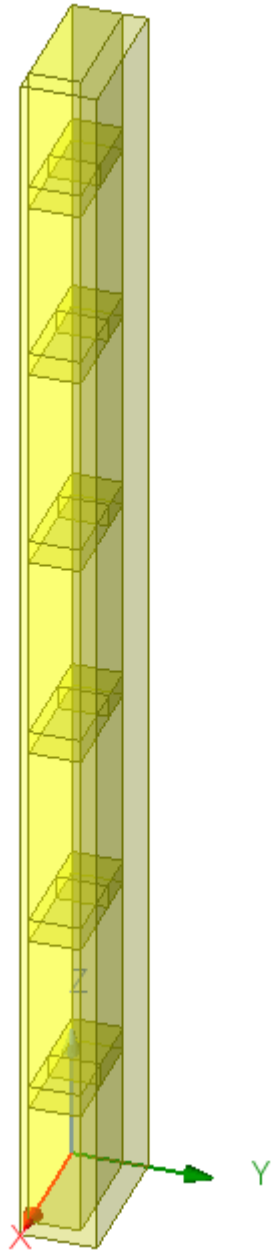

# Design Project 3

By : Nittala Satya Surya Lakshmi Vasuki Siva Srinivas

#Id – 620094

Email – [sn620094@wne.edu](mailto:sn620094@wne.edu)

1. Design a lumped element bandpass filter that meets the following performance specifications:
  - $f_0 = 22 \text{ GHz}$ .
  - $BW_f = 1 \text{ GHz}$ .
  - $RL \geq 26 \text{ dB}$  for  $f_L \leq f \leq f_H$ .
  - $IL \geq 20 \text{ dB}$  for  $f \leq f_{Ls}$  where  $f_{Ls} = 21 \text{ GHz}$ .
  - $IL \geq 35 \text{ dB}$  for  $f \geq f_{Hs}$  where  $f_{Hs} = 23.4 \text{ GHz}$ .
  - The source and load impedances of the filter are  $Z_0 = Z_0(f_0)$  (waveguide impedance). Assume that the waveguide is a WR42 waveguide ( $a = 10.6680 \text{ mm}$ ,  $b = 4.3180 \text{ mm}$ , and  $t_w = 1.0160 \text{ mm}$ ).

# Hand Calculations

## Part-1

$$a = 10.6680 \text{ mm}$$

$$b = 4.3180 \text{ mm}$$

$$t = 1 \text{ mm}$$

$$f_0 = 22 \text{ GHz}$$

$$B_{\text{Wf}} = 1 \text{ GHz}$$

$$R_L \geq 26 \text{ dB}$$

$$f_{L3} = 21 \text{ GHz}$$

$$f_{H3} = 23.4 \text{ GHz}$$

$$I_L \geq 20 \text{ dB}$$

$$I_L \geq 35 \text{ dB}$$

$$(f_H)^2 - (22)(0.0455)(f_H) - (22)^2 = 0$$

$$(f_H)^2 - (22)(0.0455)(f_H) - 484 = 0$$

$$(f_H)^2 - (f_H)(0.010) - 484 = 0$$

$$f_H = 22.5062$$

$$B_{\text{Wf}} = f_H - f_L$$

$$1 = 22.5062 - f_L$$

$$f_L = 22.5062 - 1$$

$$f_L = 21.5062$$

## Part-3

$$a = 10.6680$$

$$b = 4.3180$$

$$t_{\text{eff}} = 1.0160$$

$$f_0 = 22 \text{ GHz}$$

$$f_c = v_c / 2a$$

$$\mu = 2.997925 \times 10^8$$

$$f_c = \frac{2.997925 \times 10^8}{2 \times 10.6680 \times 10^{-3}}$$

$$f_c = 14.0510 \text{ GHz}$$

## Part-2

$$f_0 = 22 \text{ GHz}$$

$$B_{\text{Wf}} = 1 \text{ GHz}$$

$$f_0 = \sqrt{f_H f_L}$$

$$B_{\text{Wf}} = f_0 - \Delta = f_H - f_L$$

$$1 = 22 - \Delta$$

$$\Delta = 1/22 = 0.0455$$

$$\Delta = 0.0455$$

$$f_H = ?$$

$$f_L = ?$$

$$(f_H)^2 - (f_0 - \Delta) \cdot f_H - f_0^2 = 0$$

$$\lambda_{F30} = \mu_c / f_0$$

$$= \frac{2.997925 \times 10^8}{22 \times 10^9}$$

$$\lambda_{F30} = 13.6269 \text{ mm}$$

$$\lambda_{g0} = \frac{\lambda_{F30}}{\sqrt{1 - (b_c/b_0)^2}}$$

$$= \frac{13.6269}{\sqrt{1 - (14.0510/22)^2}}$$

$$= \frac{13.6269}{\sqrt{1 - (0.4079)^2}}$$

$$\lambda_{g0} = 17.7094$$

## Part-4

$$a = 10.6680$$

$$b = 4.3180$$

$$f_c = 14.0510 \text{ GHz}$$

$$\lambda_{F30} = 13.6269$$

$$\lambda_{g0} = 17.7095$$

$$M_0 = 376.7303$$

$$Z_{TE} = \frac{M_0}{\sqrt{1 - (b_c/b_0)^2}}$$

$$Z_{TE} = \frac{376.7303}{\sqrt{1 - (14.0510/22)^2}}$$

$$Z_{TE} = 376.7303$$

$$Z_{TE} = 489.5905$$

$$Z_{TE} = 489.5969$$

$$Z_0 = \left(\frac{2b}{a}\right) \cdot Z_{TE}$$

$$Z_0 = \left(\frac{2 \times 4.3180}{10.6680}\right) \times (489.5969)$$

$$Z_0 = 396.3403$$

## Part-5

$$b_L \leq b \leq b_H$$

$$R_L \geq 26 \text{ dB}$$

$$R_{\text{min}} = 26 \text{ dB}$$

$$|S_{11}^{RL}|_{\text{dB}} \leq -26$$

$$|S_{11}^{RL}|_{\text{max}} = 10^{(26/20)} = 10^{1.3} = 19.95$$

$$|S_{11}^{RL}|_{\text{max}} = 0.0501$$



$$|S_{21}^{RL}|_{\min} = \sqrt{1 - |S_{21}^{RL}|^2}$$

$$= \sqrt{1 - (0.050)^2}$$

$$|S_{21}^{RL}|_{\min} = 0.9987$$

$$|S_{21}^{RL}|_{dB} = -0.0109$$

$$AP \leq -|S_{21}|_{dB}$$

$$AP \leq 0.0109$$

$$AP = 0.0109 \text{ dB}$$

Part-6

$$f_{LS} = 21 \text{ GHz}$$

$$f_{HS} = 23.4 \text{ GHz}$$

$$IL \geq 20 \text{ dB} \rightarrow AL_S = 20 \text{ dB}$$

$$AL_S = 20 \text{ dB} \rightarrow f_{LS} = 21 \text{ GHz}$$

$$IL \geq 35 \text{ dB} \rightarrow AH_S = 35 \text{ dB}$$

$$AH_S = 35 \text{ dB} \text{ \& } f_{HS} = 23.4 \text{ GHz}$$

Part-7

$$f_L = 21.5062$$

$$f_H = 22.5062$$

$$AP = 0.0109 \text{ dB}$$

$$AP(w/w) = 10^{(AP/10)}$$

$$= 10^{(0.0109/10)}$$

$$AP(w/w) = 1.0025$$

$$XP = AP - 1$$

$$XP = 1.0025 - 1$$

$$XP = 0.0025$$

$$\epsilon = \sqrt{XP}$$

$$= \sqrt{0.0025}$$

$$= 0.05$$

$$\epsilon = 0.0502$$

Part-8

$$f_{LS} = 21 \text{ GHz}$$

$$AL_S = 20 \text{ dB}$$

$$AL_S(w/w) = 10^{(20/10)}$$

$$AL_S(w/w) = 100$$

$$X_{LS} = AL_S - 1$$

$$X_{LS} = 99 w/w$$

$$\Omega_{LS} = \left(\frac{1}{A}\right) \left[ \left( \frac{f_{LS}}{f_0} \right) - \left( \frac{f_0}{f_{LS}} \right) \right]$$

$$= \left( \frac{1}{0.0455} \right) \left[ \left( \frac{21}{22} \right) - \left( \frac{22}{21} \right) \right]$$

$$= \left( \frac{1}{0.0455} \right) \left[ (0.9545) - (1.0476) \right]$$

$$\Omega_{LS} = -2.0476$$

$$N_{LS} \geq \frac{\cosh^{-1} \left[ \left( \frac{1}{\epsilon} \right) \sqrt{X_{LS}} \right]}{\cosh^{-1} (\Omega_{LS})}$$

$$N_{LS} = 4.4514$$

$$\therefore N_{LS} = 5$$

Part-9

$$f_{HS} = 23.4 \text{ GHz}$$

$$AH_S = 35 \text{ dB}$$

$$AH_S = 10^{(AH_S/10)}$$

$$= 10^{(35/10)}$$

$$AH_S = 3162.2776 w/w$$

$$X_{HS} = AH_S - 1$$

$$X_{HS} = 3161.2776 w/w$$

$$\Omega_{HS} = \left(\frac{1}{A}\right) \left[ \left( \frac{f_{HS}}{f_0} \right) - \left( \frac{f_0}{f_{HS}} \right) \right]$$

$$= \left( \frac{1}{0.0455} \right) \left[ \left( \frac{23.4}{22} \right) - \left( \frac{22}{23.4} \right) \right]$$

$$= \left( \frac{1}{0.0455} \right) \left[ (1.0636) - (0.940) \right]$$

$$= 2.7162$$

$$\Omega_{HS} = 2.7162$$

$$N_{HS} \geq \frac{\cosh^{-1} \left[ \left( \frac{1}{\epsilon} \right) \sqrt{X_{HS}} \right]}{\cosh^{-1} (\Omega_{HS})}$$

$$N_{HS} = 4.6568$$

$$N_{HS} = 5$$

Part-10

$$NP = 5$$

$$\therefore \text{No. of Branches} = NP$$

$$= 5$$

$$\text{No. of lines} = 5 + 1 = 6$$

$$N_{lines} = 6$$

$$N_{resonator} = \text{No. of Branches}$$

$$N_{resonator} = 5$$

$$\text{Chebyshev } 0.01 \text{ dB}$$

$$\text{Ripple } 5^{\text{th}} \text{ order}$$

$$g_0 = 1$$

$$g_1 = 0.7563$$

$$g_2 = 1.3049$$

$$g_3 = 1.5773$$

$$g_4 = 1.3049$$

$$g_5 = 0.7563$$

$$g_6 = 1.000$$

## MATLAB Calculations

```
f0 = 22.0000 GHz
Bwf = 1.0000 GHz
fL = 21.5000 GHz
fH = 22.5000 GHz
delta = 0.0455
S21_min (RL) = 0.9987 W/W
S21_min (RL) = -0.0109 dB
Ap (RIPPLE) = 0.0109 dB
fc = 14.0510 GHz
lambda_fs0 = 13.6269 mm
lambda_g0 = 17.7095 mm
ZTE = 489.5969 Ohms
Z0 = 396.3403 Ohms
NLS = 4.4514
NHS = 4.6568
w0 = 138.2301 Grad/s
```

-----  
C1 = 303.7008 fF

L1 = 172.3253 pH

L2 = 82.3125 nH

C2 = 635.8128 aF

C3 = 633.3826 fF

L3 = 82.6283 pH

L4 = 82.3125 nH

C4 = 635.8128 aF

C5 = 303.7008 fF

L5 = 172.3253 pH  
-----

-----  
lambda\_fs = 13.9438 mm

lambda\_g\_fL = 18.4224 mm

lambda\_fs\_f0 = 13.6269 mm

lambda\_g\_f0 = 17.7095 mm

lambda\_fs\_fH = 13.3241 mm

lambda\_g\_fH = 17.0596 mm

Delta\_Lambda = 0.0770  
-----

-----  
K01\_Z0 = 0.3998

K12\_Z0 = 0.1217


K23\_Z0 = 0.0843


K34\_Z0 = 0.0843

K45\_Z0 = 0.1217


K56\_Z0 = 0.3998  
\\

# MATLAB Ideal Lumped Elements

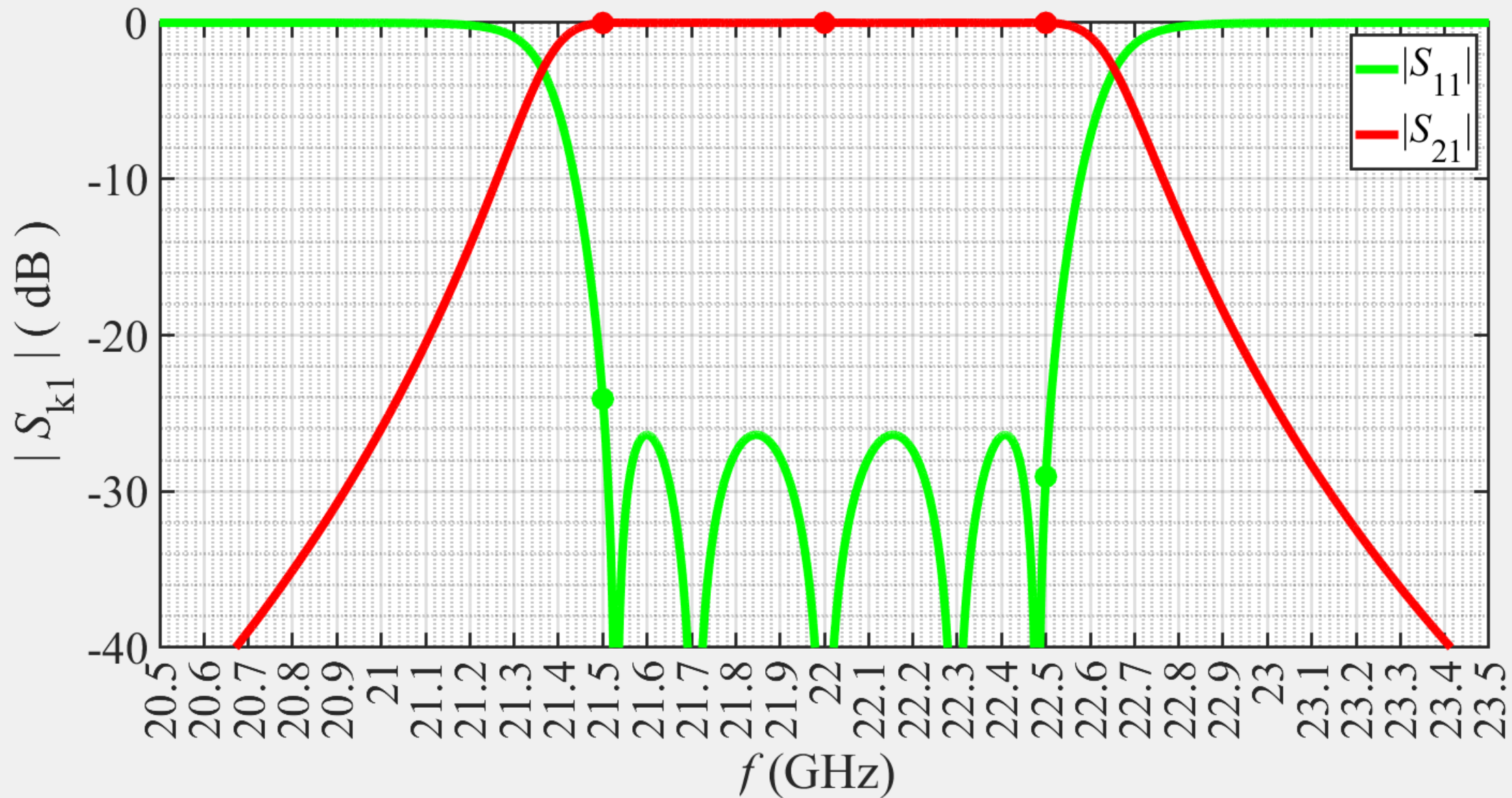

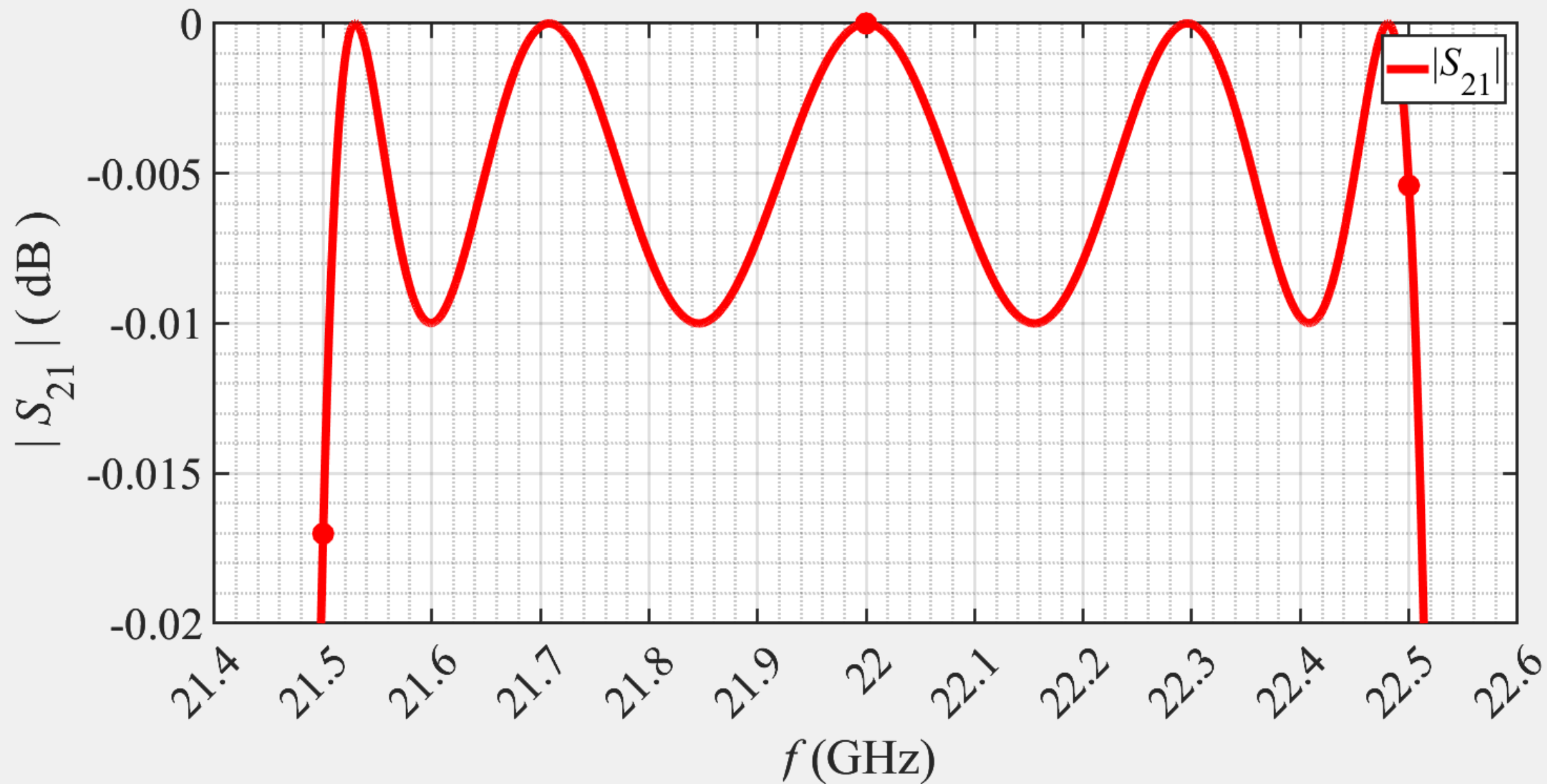

# Waveguide inductive iris BPF Design

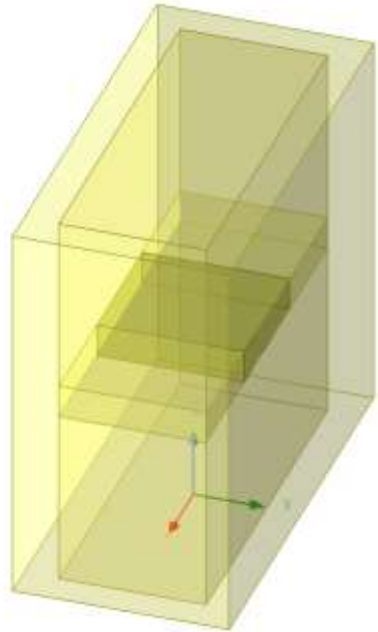


**BPF Full Model Iris Sweep**

Properties				
Name	Value	Unit	Evaluated Value	Type
a	10.668	mm	10.668mm	Design
b	4.318	mm	4.318mm	Design
tw	1.016	mm	1.016mm	Design
t_iris	1	mm	1mm	Design
dp	$(1/2)*a$		5.334mm	Design
L	$2*dp+t\_iris$		11.668mm	Design
ag_0	4	mm	4mm	Design
aw	$a+2*tw$		12.7mm	Design
bw	$b+2*tw$		6.35mm	Design


Setup Sweep Analysis		
Sweep Definitions		
Sync #	Variable	Description
	ag_0	Linear Step from 0.25mm to 6.5mm, step=0.25mm

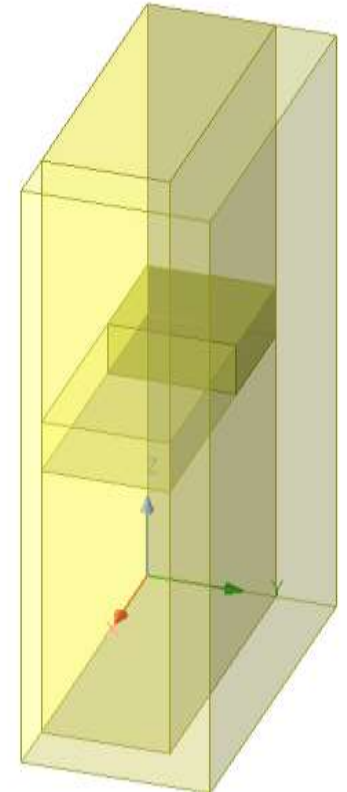


**BPF Quarter Model Iris Sweep**


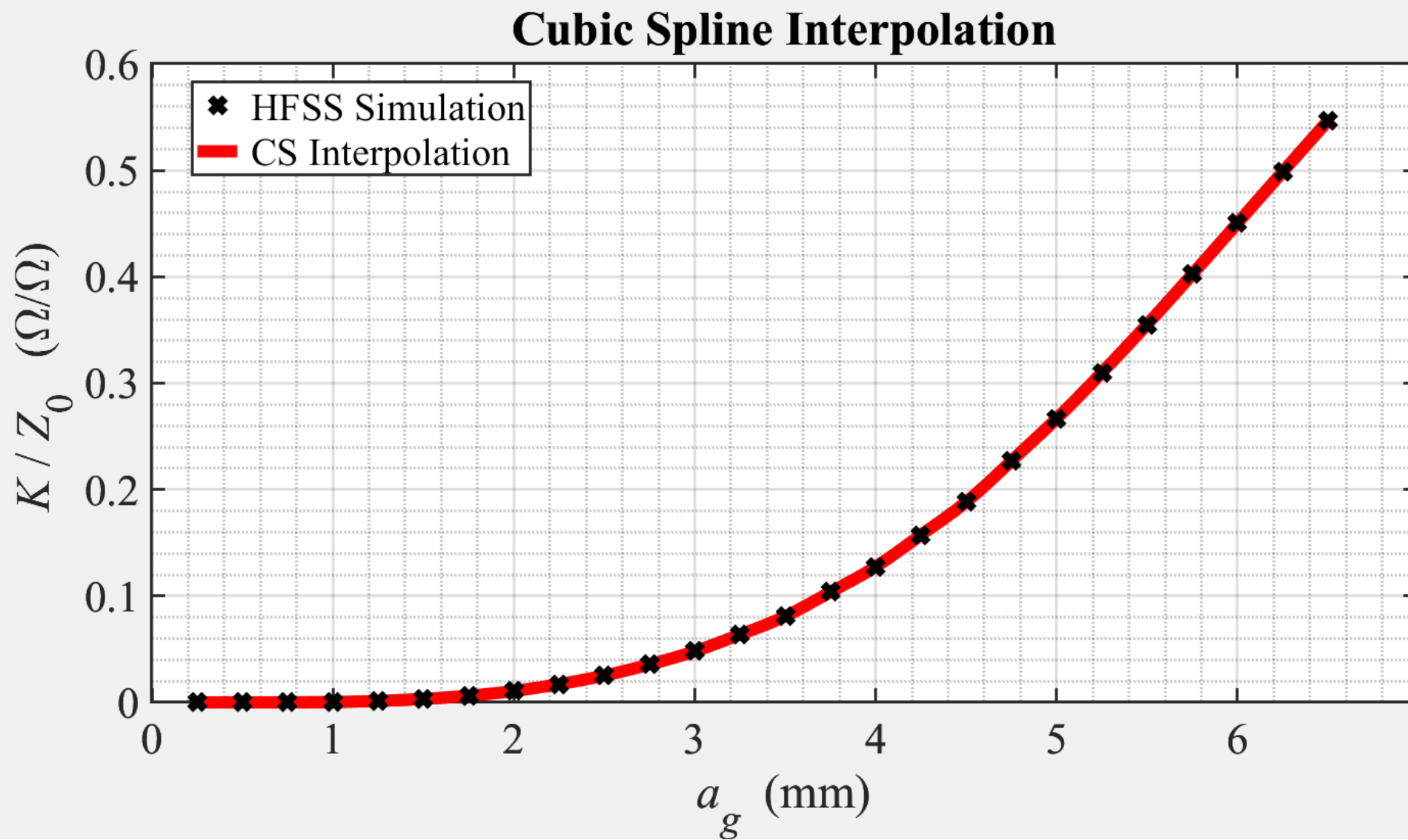
# Iris Sweep - Cubic spline Interpolation





# WG iris BPF HFSS (PEC)

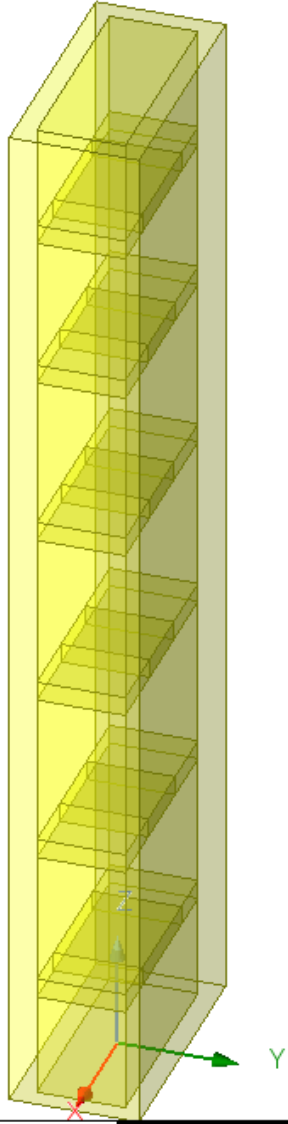

BPF iris Full Model Pec


Name	Value	Unit	Evaluated Value	Type
a	10.668	mm	10.668mm	Design
b	4.318	mm	4.318mm	Design
tw	1.016	mm	1.016mm	Design
t	1	mm	1mm	Design
ag	[0, 5.737, 3.9424, 3.5427, 3.9424, 5.737, 0]	mm	[0, 5.737, 3.942...	Design
zk	[0, 5.334, 13.1594, 21.9746, 30.9249, 39.7401, 47.5655, 53.8995]	mm	[0, 5.334, 13.15...	Design
L	53.8995	mm	53.8995mm	Design
dp	$(1/2)*a$		5.334mm	Design
aw	$a+2*tw$		12.7mm	Design
bw	$b+2*tw$		6.35mm	Design

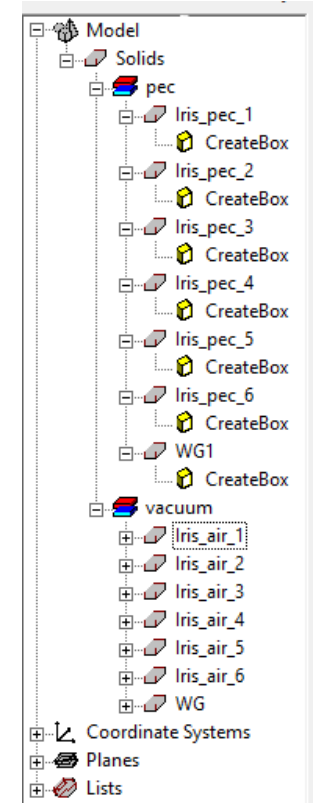

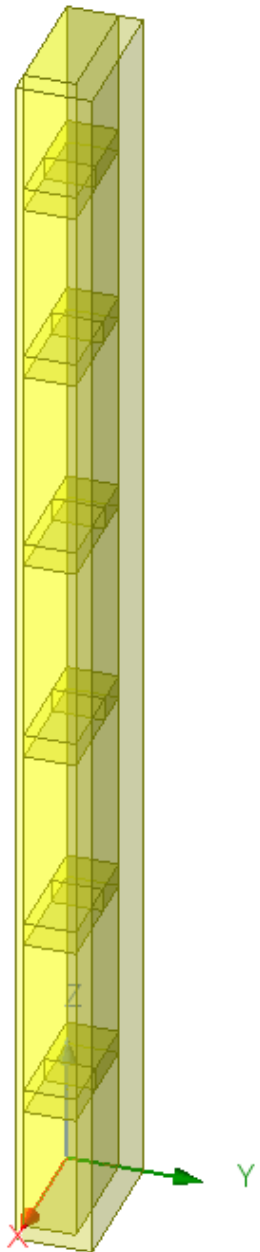


Name	Value	Unit	Evaluated Value	Type	
a	10.668	mm	10.668mm	Design	
b	4.318	mm	4.318mm	Design	
tw	1.016	mm	1.016mm	Design	
t	1	mm	1mm	Design	
ag	[0, 5.737, 3.9424, 3.5427, 3.5427, 3.9424, 5.737, 0]	mm	[0, 5.737, 3.942...	Design	
zk	[0, 5.334, 13.1594, 21.9746, 30.9249, 39.7401, 47.5655, 53.8995]	mm	[0, 5.334, 13.15...	Design	
L	53.8995	mm	53.8995mm	Design	
dp	$(1/2)*a$		5.334mm	Design	
aw	$a+2*tw$		12.7mm	Design	
bw	$b+2*tw$		6.35mm	Design	

**BPF iris Quarter Model Pec**

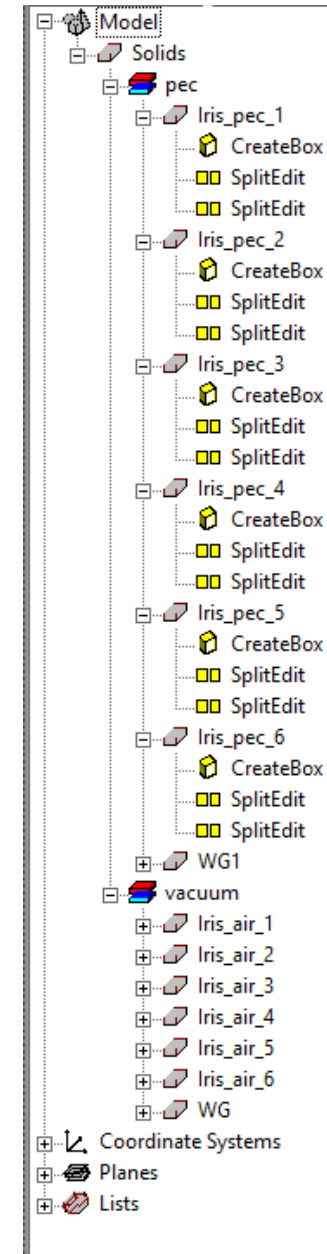





# WG iris BPF HFSS (PEC) $|S_{11}|$ and $|S_{21}|$

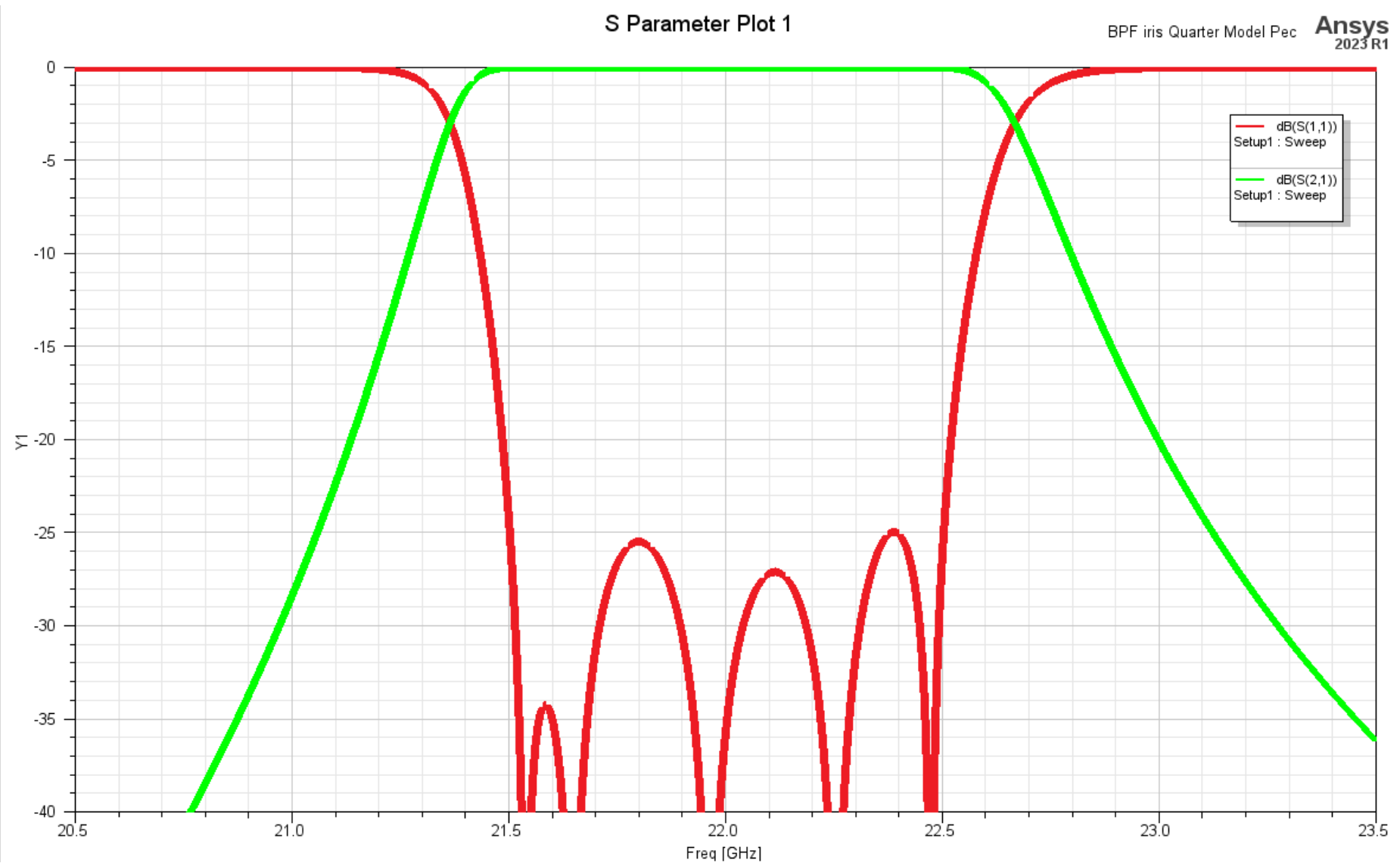

# WG iris BPF HFSS (PEC) $|S_{21}|$

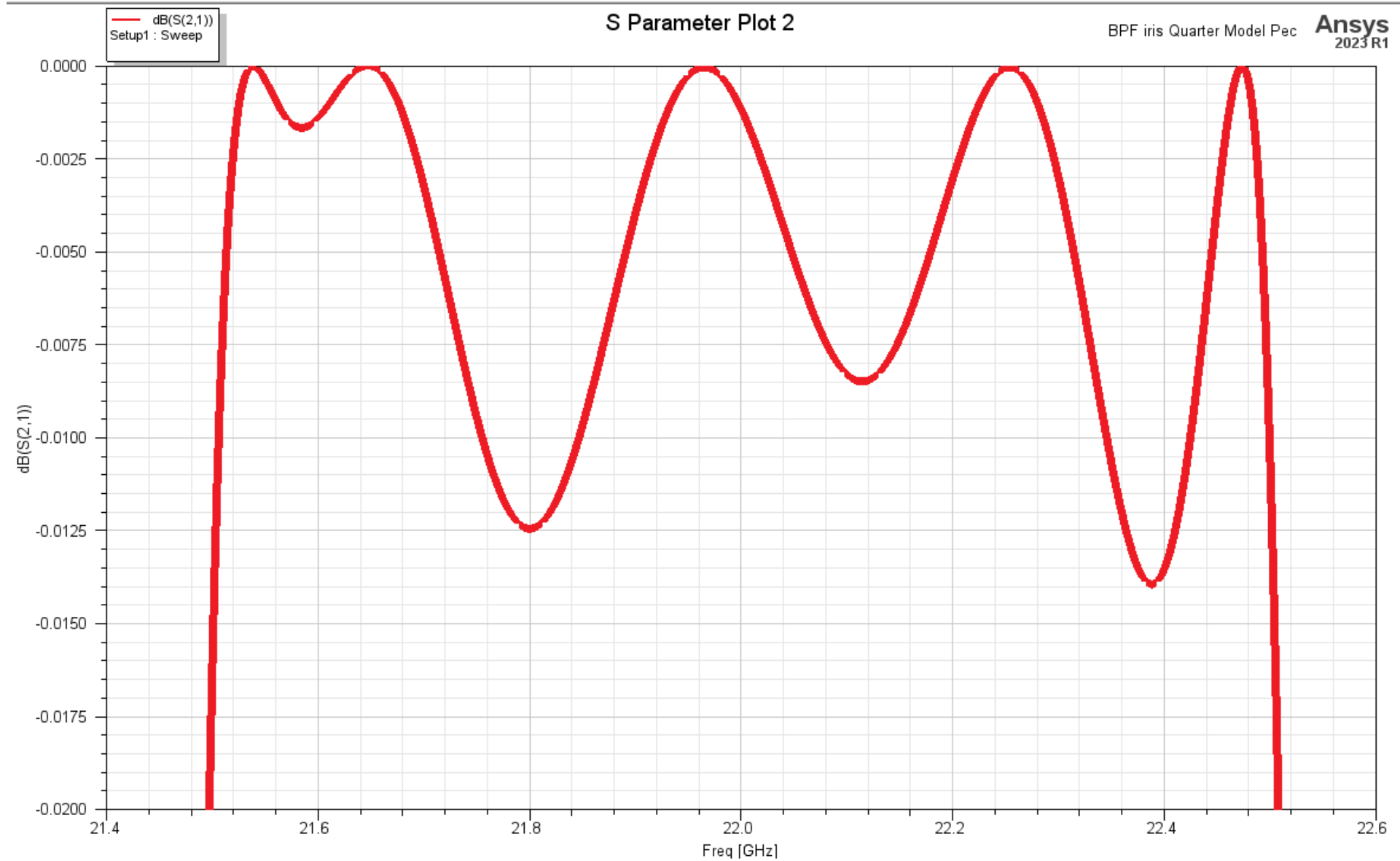



# WG iris BPF HFSS (Copper(Loss))

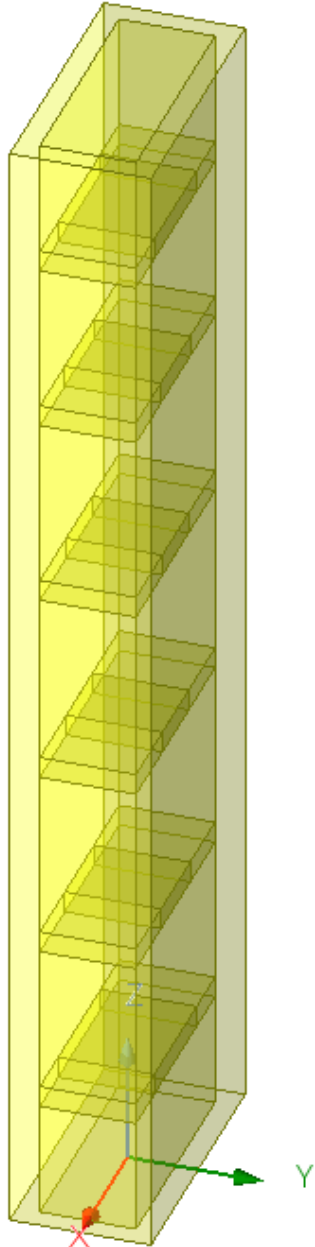

Name	Value	Unit	Evaluated Value	Type
a	10.668	mm	10.668mm	Design
b	4.318	mm	4.318mm	Design
tw	1.016	mm	1.016mm	Design
t	1	mm	1mm	Design
ag	[0, 5.737, 3.9424, 3.5427, 3.5427, 3.9424, 5.737, 0]	mm	[0, 5.737, 3.942...	Design
zk	[0, 5.334, 13.1594, 21.9746, 30.9249, 39.7401, 47.5655, 53.8995]	mm	[0, 5.334, 13.15...	Design
L	53.8995	mm	53.8995mm	Design
dp	(1/2)*a		5.334mm	Design
aw	a+2*tw		12.7mm	Design
bw	b+2*tw		6.35mm	Design


**BPF iris Full Model Copper**

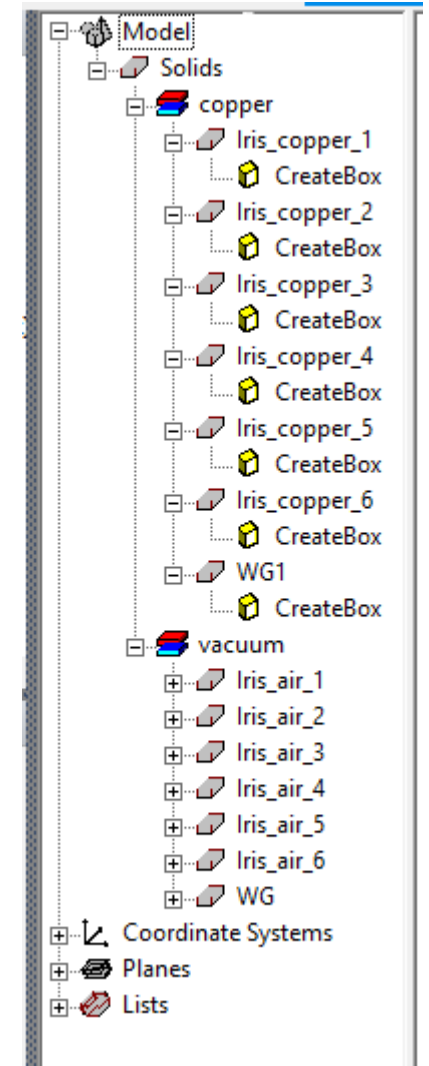

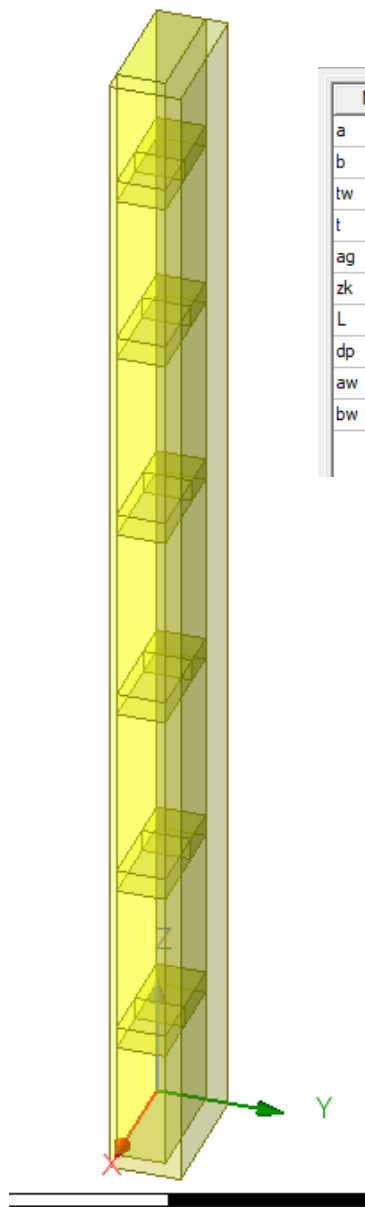


Name	Value	Unit	Evaluated Value	Type
a	10.668	mm	10.668mm	Design
b	4.318	mm	4.318mm	Design
tw	1.016	mm	1.016mm	Design
t	1	mm	1mm	Design
ag	[0, 5.737, 3.9424, 3.5427, 3.5427, 3.9424, 5.737, 0]	mm	[0, 5.737, 3.942...	Design
zk	[0, 5.334, 13.1594, 21.9746, 30.9249, 39.7401, 47.5655, 53.8995]	mm	[0, 5.334, 13.15...	Design
L	53.8995	mm	53.8995mm	Design
dp	$(1/2)*a$		5.334mm	Design
aw	$a+2*tw$		12.7mm	Design
bw	$b+2*tw$		6.35mm	Design


**BPF iris Quarter Model Copper**

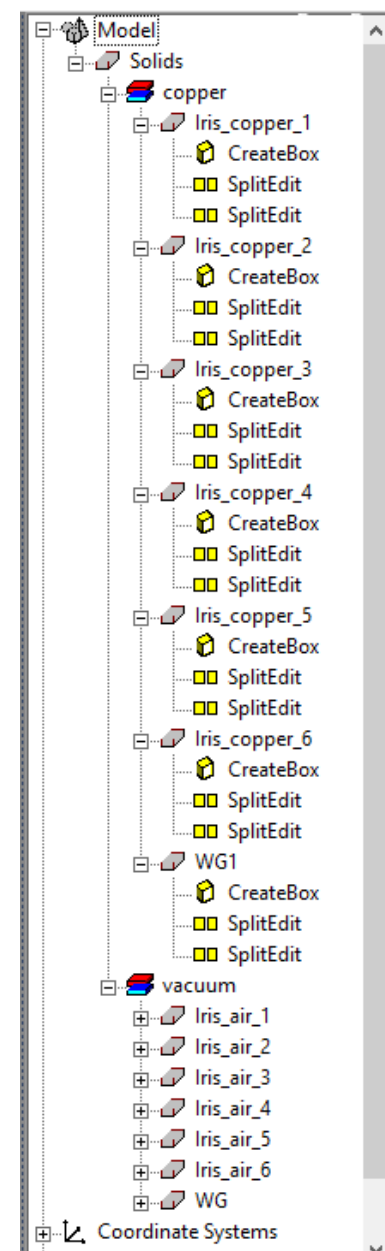

# WG iris BPF HFSS (Copper(Loss)) $|S_{11}|$ and $|S_{21}|$

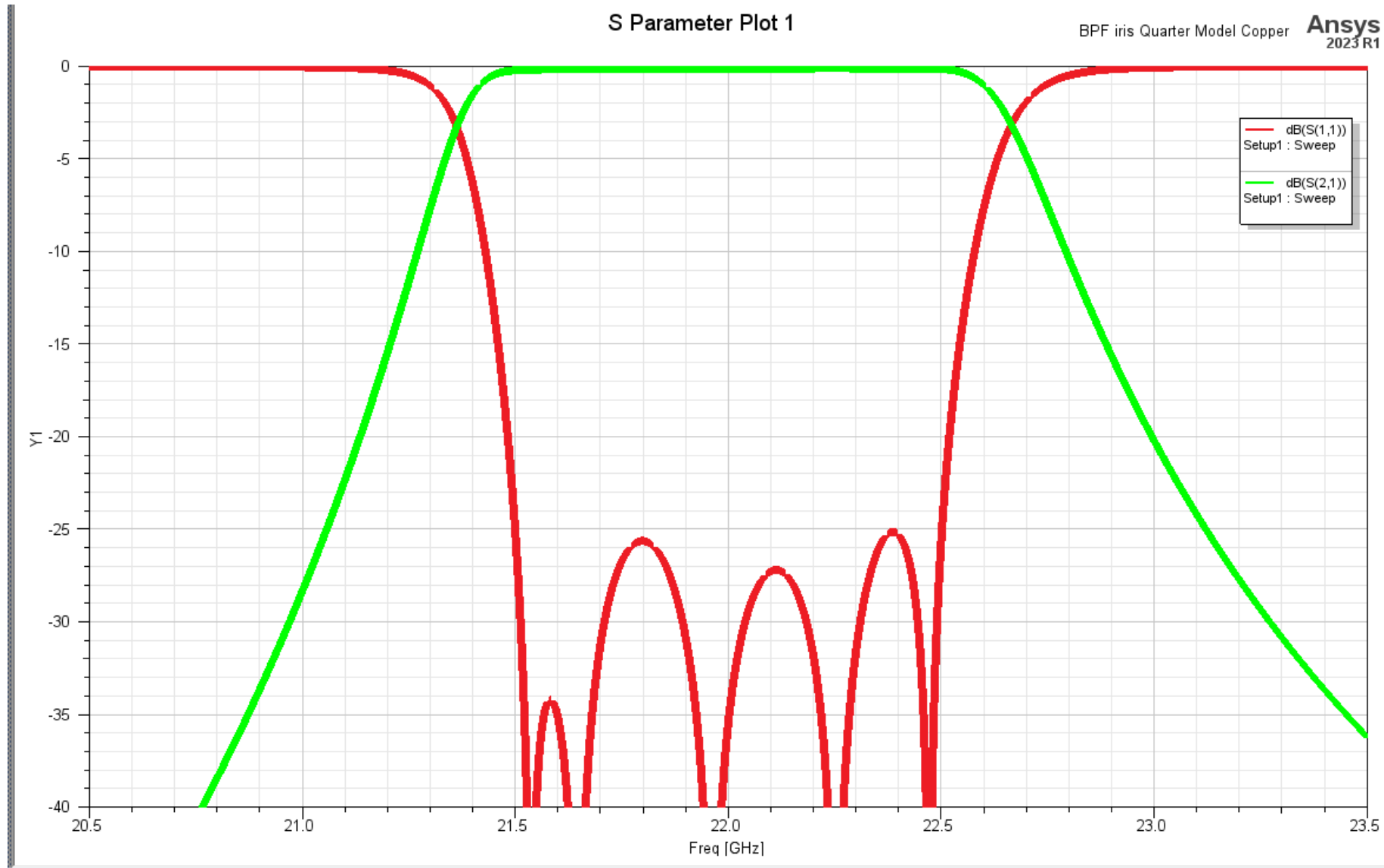


# WG iris BPF HFSS (Copper(Loss)) $|S_{21}|$

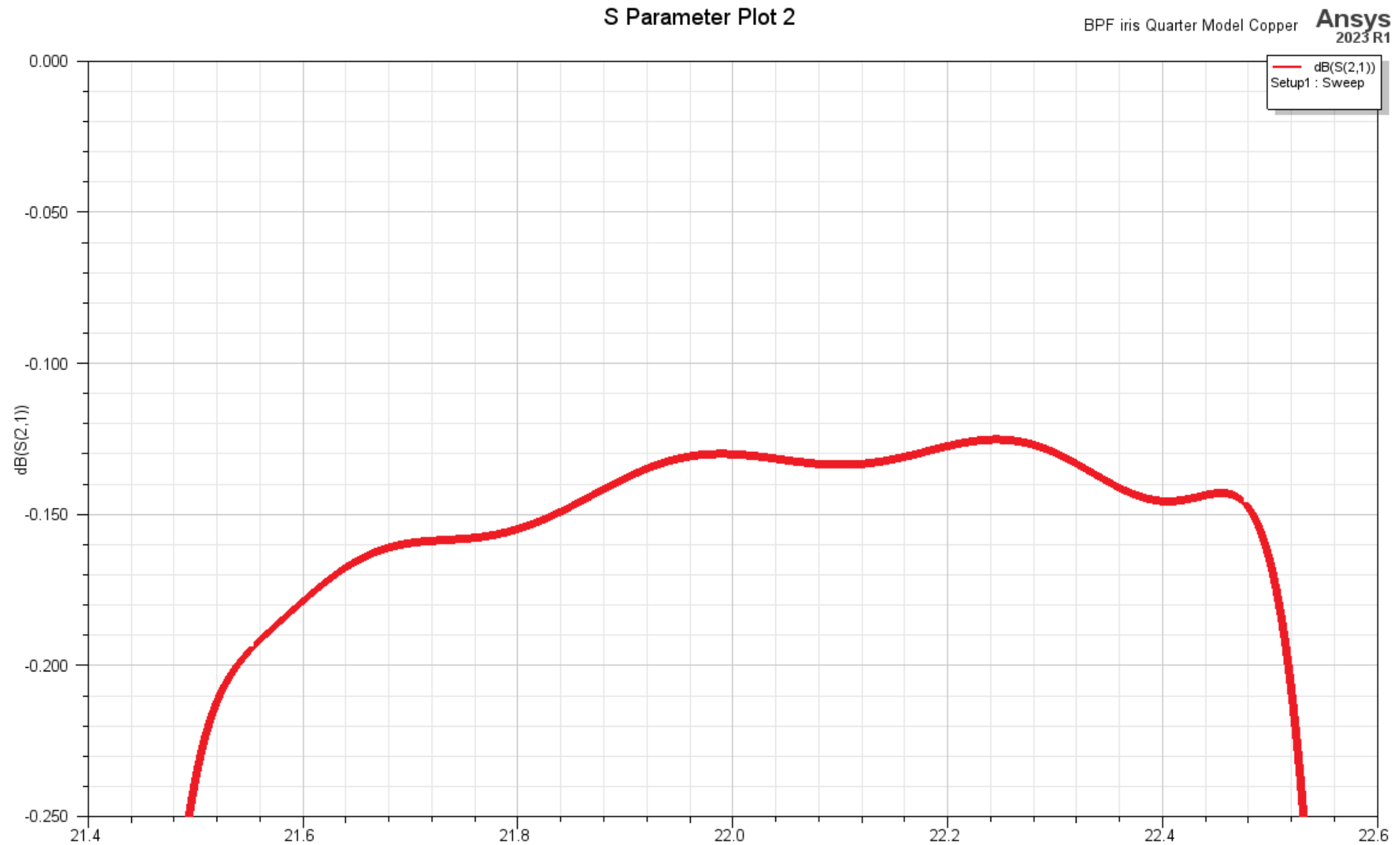


## Summary of the outcomes.

On the same graph, plot  $|S_{21}|$  in dB, for the three cases. Employ a frequency range of 20.5 GHz to 23.5 GHz and a range of -40 dB to 0 dB for  $|S_{21}|$ .

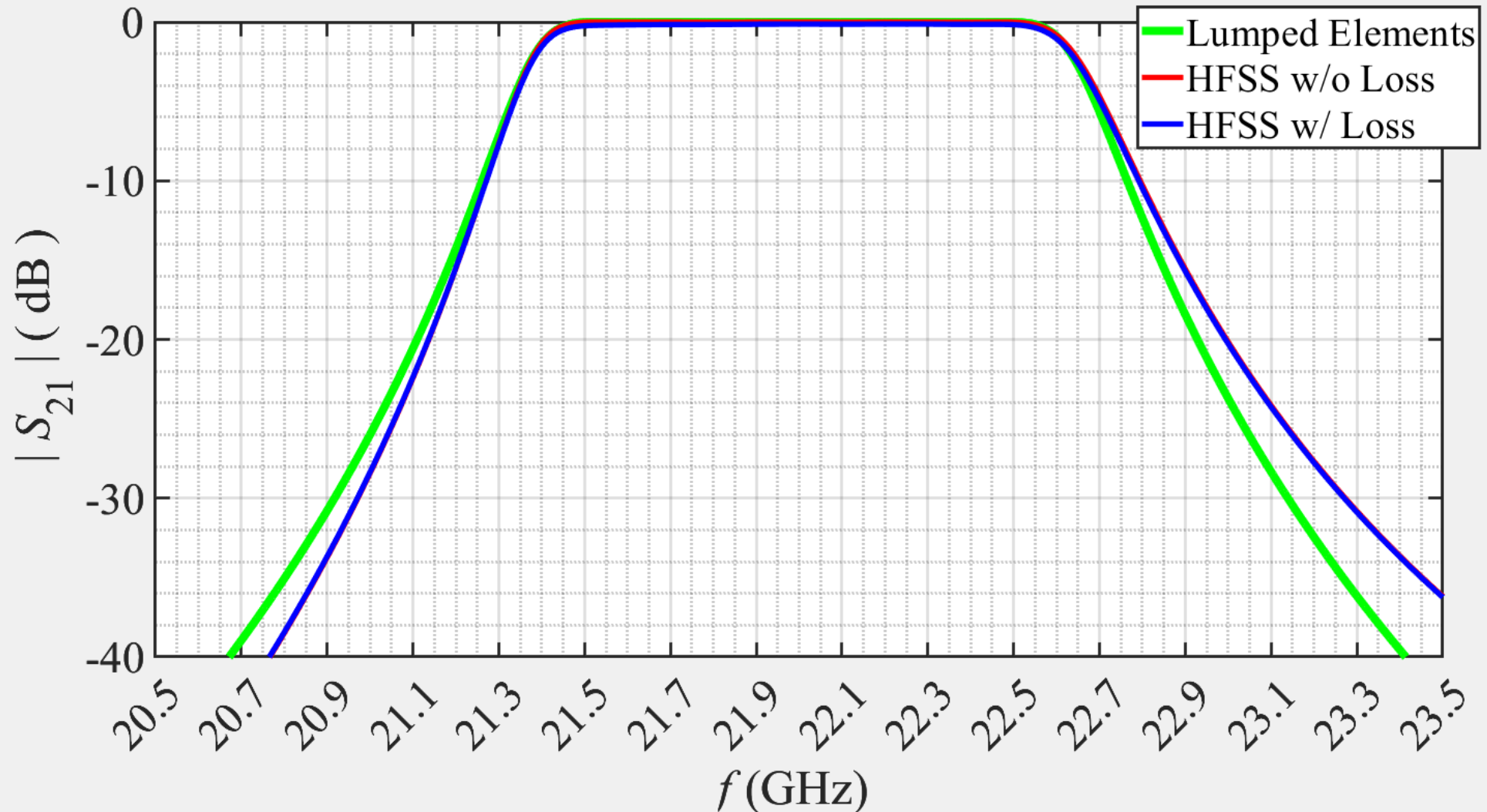


On the same graph, plot  $|S_{21}|$  in dB, for the three cases. Employ a of frequency range 21.4 GHz to 22.6 GHz and a range of -0.25 dB to 0 dB for  $|S_{21}|$ .

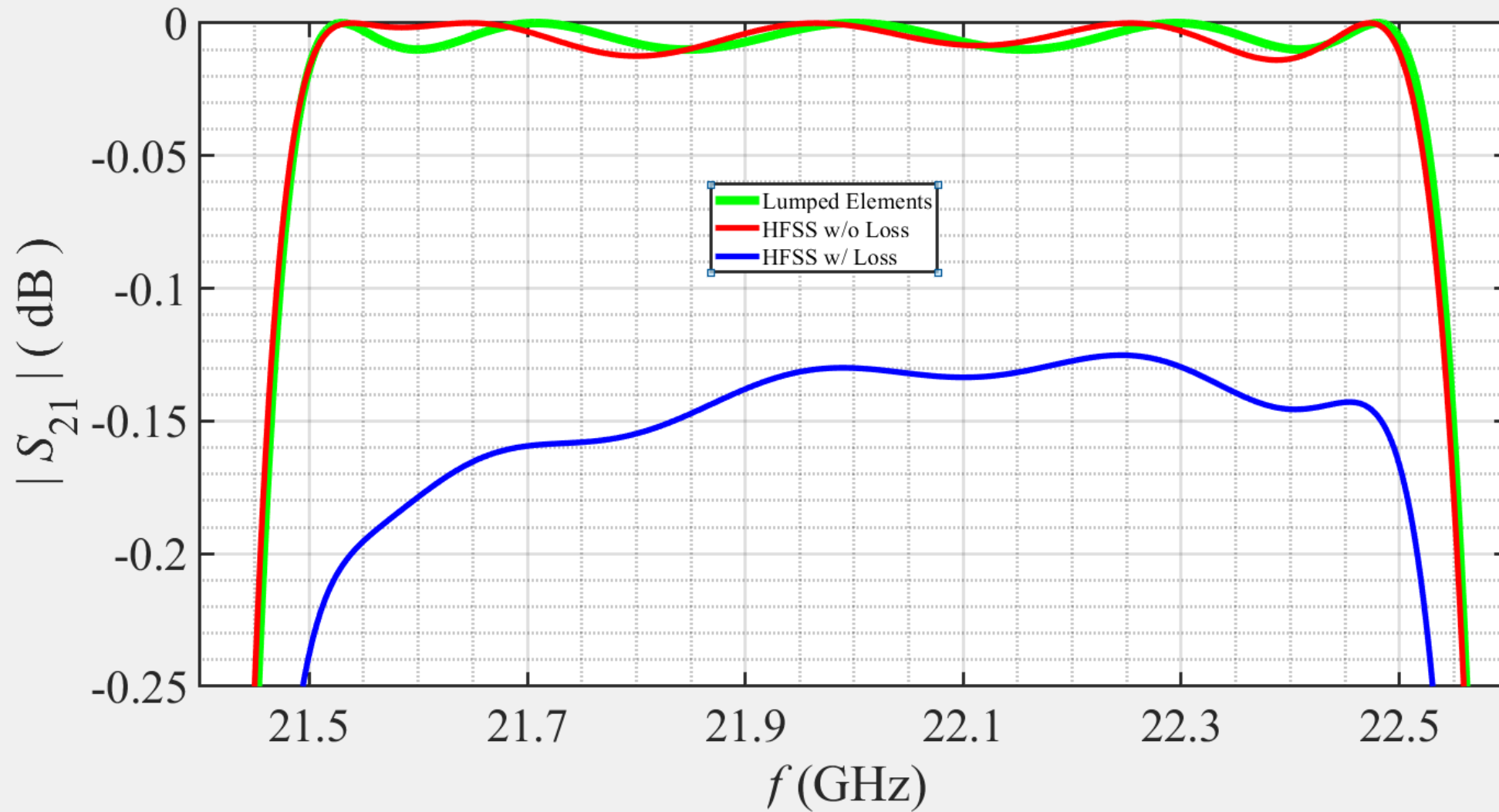



On the same graph, plot  $|S_{11}|$  in dB, for the three cases. Employ a frequency range of 21.4 GHz to 22.6 GHz and a range of -40 dB to 0 dB for  $|S_{11}|$ .

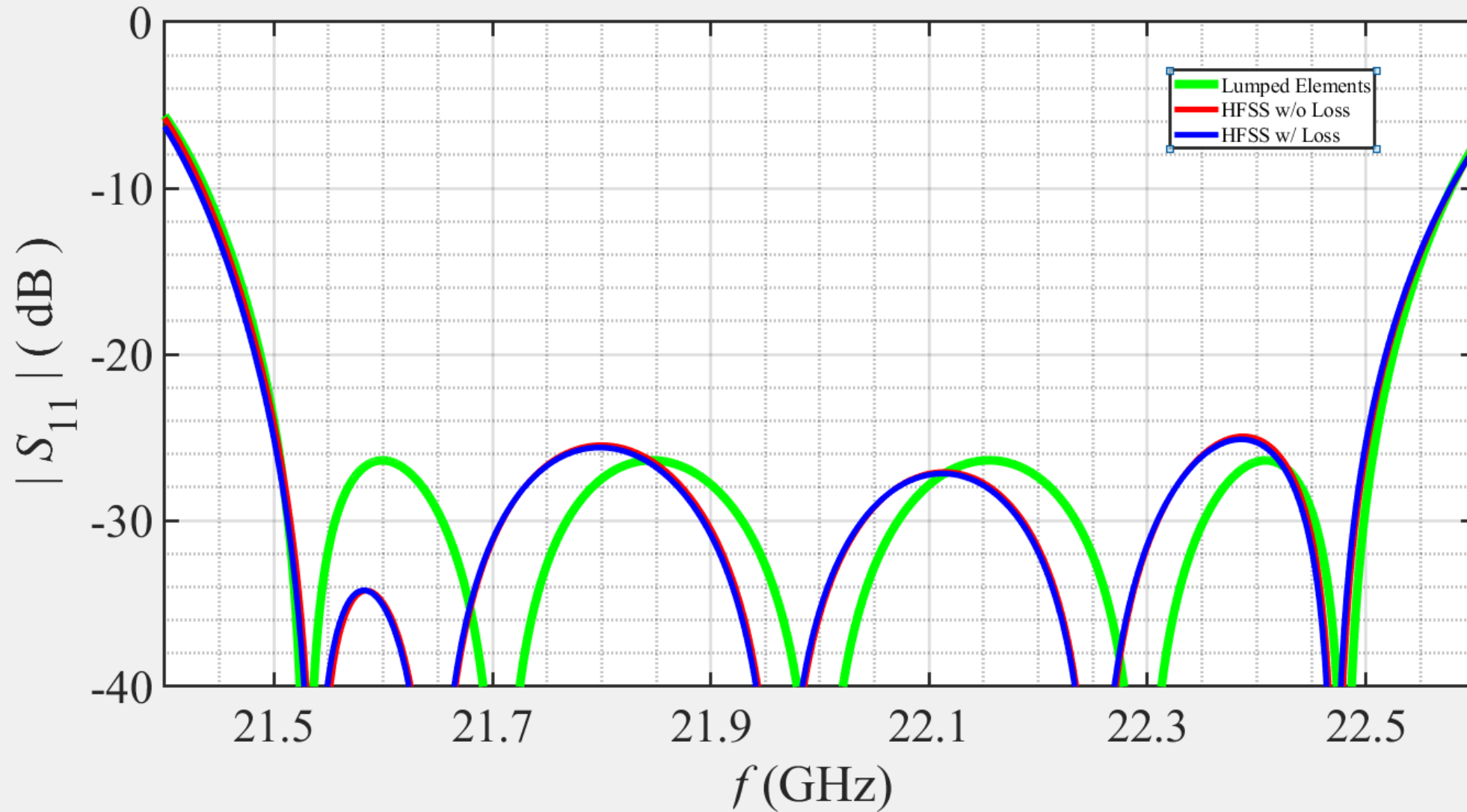

**Table 01**

k,k+1	01	12	23	34	45	56	
$K_{k,k+1}/Z_0$	0.3998	0.1217	0.0843	0.0843	0.1217	0.3998	$\Omega/\Omega$
$X_{p(k,k+1)}/Z_0$	0.5538	0.1270	0.0867	0.0867	0.1270	0.5538	$\Omega/\Omega$
$X_{s(k,k+1)}/Z_0$	0.1321	0.0876	0.0763	0.0763	0.0876	0.1321	$\Omega/\Omega$
$\Psi_{k,k+1}$	7.5244	5.0091	4.3654	4.3654	5.0091	7.5244	$^\circ$
$\emptyset_{k,k+1}$	-58.6319	-23.8746	-18.3867	-18.3867	-23.8746	-58.6319	$^\circ$
$a_g$	5.737	3.9424	3.5427	3.5427	3.9424	5.737	mm

**Table 02**

k	1	2	3	4	5	
$\theta_{k,k+1}$	138.7467	158.8693	161.6133	158.8693	138.7467	°
$d_k/\lambda_{g0}$	0.3854	0.4413	0.4489	0.4413	0.3854	$\Omega/\Omega$
$d_k$	6.8254	7.8153	7.9502	7.8153	6.8254	mm

## Appendices

- HFSS
- MATLAB
- MS Excel

THE END